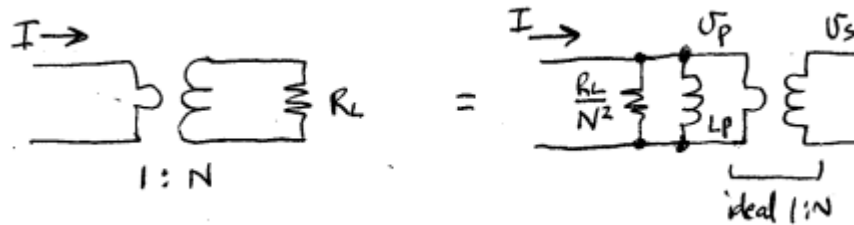


# Current Transformers

G. Barrere – Exality Corporation

Measuring AC current  $I$  as a voltage across known resistance  $R_L$ .



The normal transformer model pertains, but primary inductance  $L_p$  is very small.  $R_L$  may be reflected to the primary as shown above, so  $v_p$  has a highpass characteristic with cutoff frequency of

$$f_1 = \frac{R_L}{2 \cdot \pi \cdot L_p \cdot N^2}$$

Above  $f_1$ ,  $v_p = \frac{I \cdot R_L}{N^2}$  and  $v_s = v_p \cdot N = \frac{I \cdot R_L}{N}$ , assuming no losses and perfect coupling.

## High frequency cutoff


If  $R_L$  is replaced by  $Z_L = R_L \parallel C_S$  a lowpass pole is created by  $R_L$  and  $C_S$  with cutoff frequency

$$f_2 = \frac{1}{2 \cdot \pi \cdot R_L \cdot C_S}$$

$C_S$  may be due to secondary winding or load capacitance. Reflected to the primary this load is  $\frac{Z_L}{N^2}$

which does not change cutoff frequency with  $N$ . As  $N$  increases  $C_S$  will also increase somewhat because of increased winding capacitance, but this increased  $C_S$  is the only thing which affects  $f_2$ .

## Trends with N variation

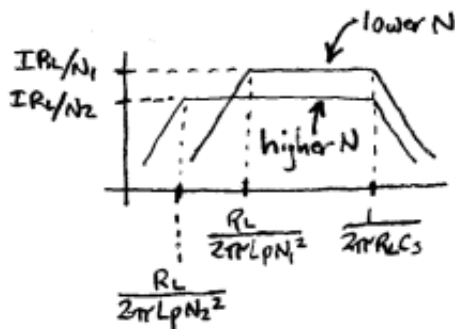

Here is the variation in transformer output voltage with changing  $N$ . As  $N$  goes up the insertion impedance, output voltage, and highpass cutoff frequency  $f_1$  all go down.